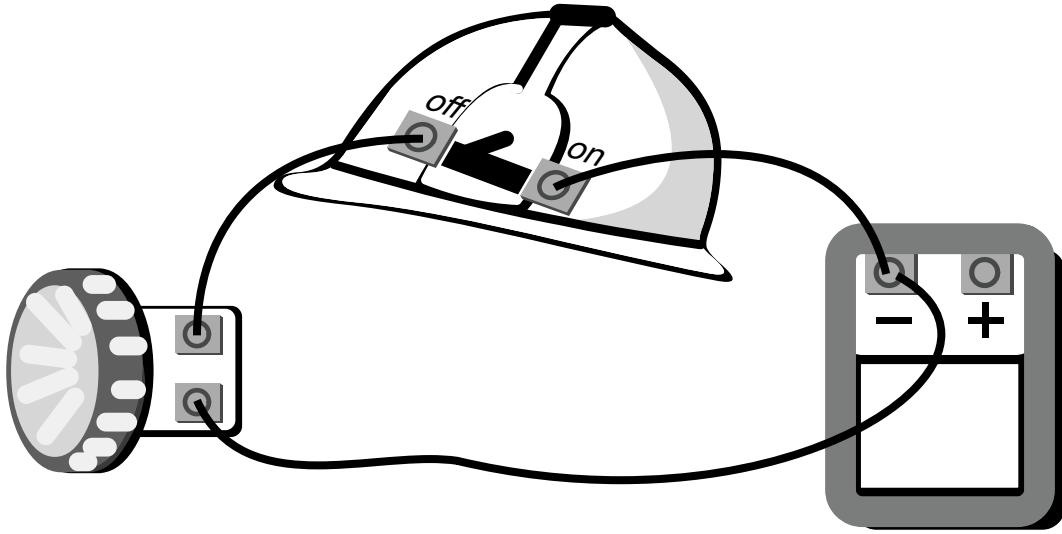



Which circuit lights the Cap Lamp?

Name _____




Yes

No

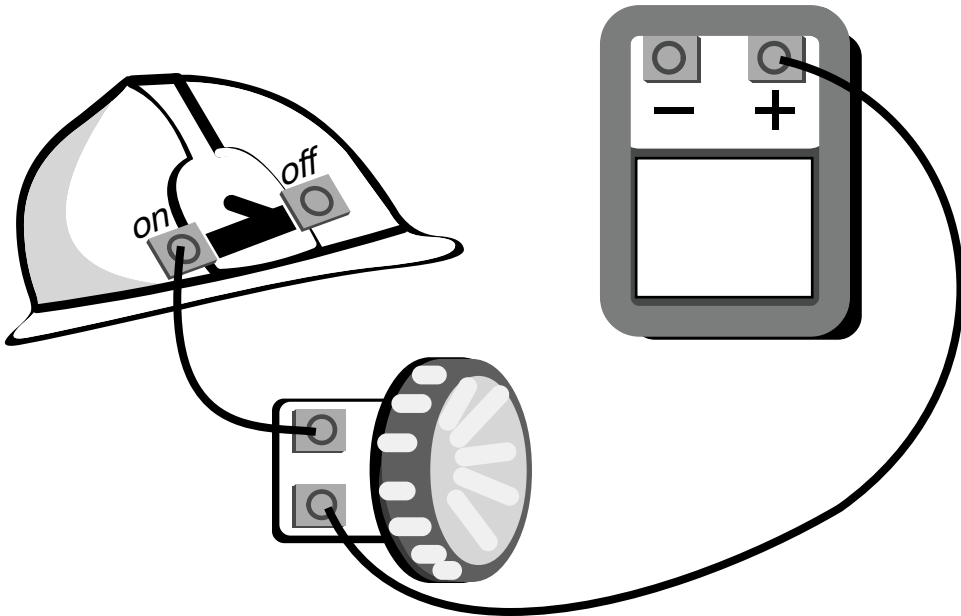

Yes

No

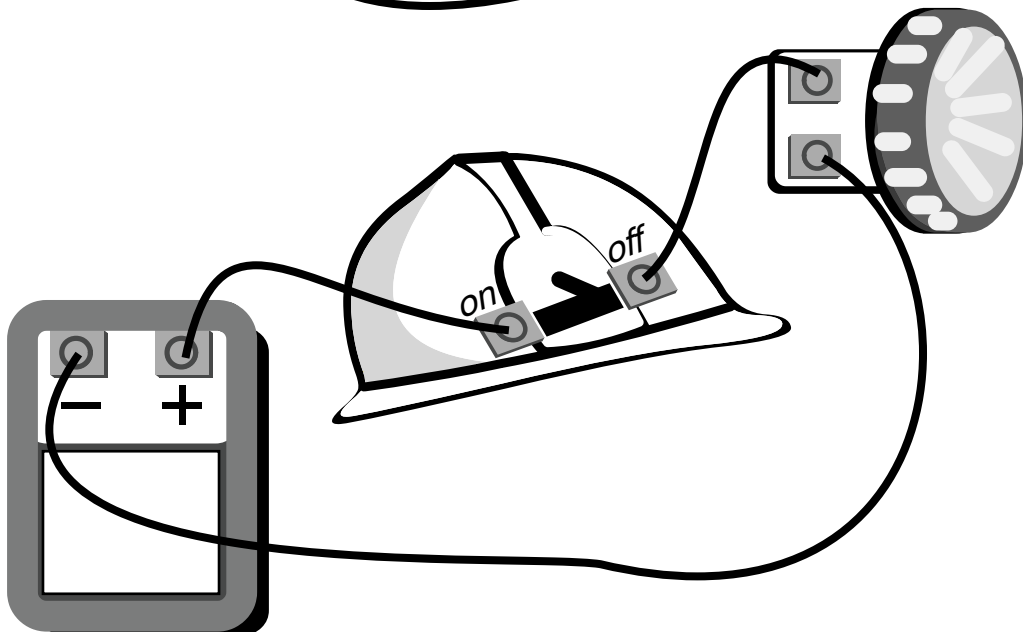

Yes

No